

Tigran Kurkchigants

ENGR 378.04

Pre-lab 3

1.

G	D	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


Output depends on the enable signal G and input signal D. When the latch is not enabled (i.e. $G=0$), the output is in retention state (i.e. keeps its previous output). When $G=1$, output follows the input signal D.

The FF is triggered by the falling edge of the clock. J acts as 'set' & K acts as 'reset'. When both J & K are zero, FF does not change its state. When both J & K are one, the output is toggled.

2.

Present state	Next state		J _A		K _A		J _B		K _B	
	X=0	X=1	X=0	X=1	X=0	X=1	X=0	X=1	X=0	X=1
00	01	00	0	0	0	0	1	0	0	0
			0	0	1	1	1	0	1	1
01	10	00	1	0	0	0	0	0	1	1
			1	0	1	1	1	1	1	1
10	11	00	0	0	0	1	1	0	0	0
			1	1	0	1	1	0	1	1
11	00	00	0	0	1	1	0	0	1	1
			1	1	1	1	1	1	1	1

Present state	Next state		J_A		K_A		J_B		K_B	
	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$
00	01	00	0	0	X	X	1	0	X	X
01	10	00	1	0	X	X	X	X	1	1
10	11	00	X	X	0	1	1	0	X	X
11	00	00	X	X	1	1	X	X	1	1

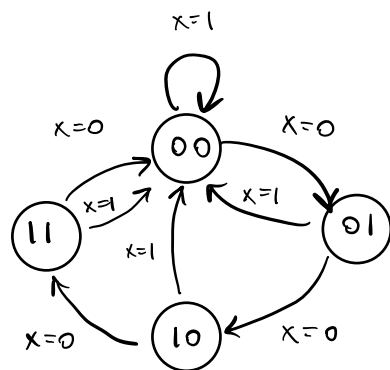

$Q_A Q_B$	x			
	00	01	11	10
0	0	1	X	X
1	0	0	X	X

$$J_A = Q_B x'$$

$Q_A Q_B$	x			
	00	01	11	10
0	X	X	1	0
1	X	X	1	1

$$K_A = Q_B + x$$

$Q_A Q_B$	x			
	00	01	11	10
0	1	X	X	1
1	0	X	X	0

$$J_B = x'$$

$Q_A Q_B$	x			
	00	01	11	10
0	X	1	1	X
1	X	1	1	X

$$K_B = Q_B$$

